

Chapter Assessment

Section 1 Currents and Circuits: Mastering Problems

54. **Lightbulbs** A current of 1.2 A is measured through a lightbulb when it is connected across a 120-V source. At what rate does the bulb transform energy? (Level 1)

SOLUTION:

$$P = IV = (1.2 \text{ A})(120 \text{ V}) = 1.4 \times 10^2 \text{ W}$$

ANSWER:

$$P = 1.4 \times 10^2 \text{ W}$$

62. What voltage is applied to a 4.0- Ω resistor if the current is 1.5 A? (Level 1)

SOLUTION:

$$V = IR = (1.5 \text{ A})(4.0 \Omega) = 6.0 \text{ V}$$

ANSWER:

$$V = 6.0 \text{ V}$$

64. A voltage of 75 V is placed across a 150- Ω resistor. What is the current through the resistor? (Level 1)

SOLUTION:

$$V = IR$$

$$I = \frac{V}{R} = \frac{75 \text{ V}}{150 \Omega} = 5.0 \text{ A}$$

ANSWER:

$$I = 5.0 \text{ A}$$

Section 1 Simple Circuits: Practice Problems

1. Three $22\text{-}\Omega$ resistors are connected in series across a 125-V generator. What is the equivalent resistance of the circuit? What is the current in the circuit?

SOLUTION:

$$\begin{aligned} R &= R_1 + R_2 + R_3 \\ &= 22\ \Omega + 22\ \Omega + 22\ \Omega \\ &= 66\ \Omega \\ I &= \frac{\Delta V}{R} = \frac{125\ \text{V}}{66\ \Omega} = 2.9\ \text{A} \end{aligned}$$

ANSWER:

$$R = 66\ \Omega, I = 2.9\ \text{A}$$

2. A $12\text{-}\Omega$, a $15\text{-}\Omega$, and a $5\text{-}\Omega$ resistor are connected in a series circuit with a 75-V battery. What is the equivalent resistance of the circuit? What is the current in the circuit?

SOLUTION:

$$\begin{aligned} R &= R_1 + R_2 + R_3 \\ &= 12\ \Omega + 15\ \Omega + 5\ \Omega = 32\ \Omega \\ I &= \frac{\Delta V}{R} = \frac{75\ \text{V}}{32\ \Omega} = 2.3\ \text{A} \end{aligned}$$

ANSWER:

$$R = 32\ \Omega, I = 2.3\ \text{A}$$

4. A 9-V battery is in a circuit with three resistors connected in series.

- If the resistance of one of the resistors increases, how will the equivalent resistance change?
- What will happen to the current?
- Will there be any change in the battery voltage?

SOLUTION:

- a. It will increase.

- b. $I = \frac{\Delta V}{R}$, so it will decrease.

- c. No. It does not depend on the resistance.

ANSWER:

- a. It will increase.

- b. $I = \frac{\Delta V}{R}$, so it will decrease.

- c. No. It does not depend on the resistance.

Chapter 23 Practice Problems, Review, and Assessment

5. **CHALLENGE** Calculate the potential differences across three resistors, 12- Ω , 15- Ω , and 5- Ω , that are connected in series with a 75-V battery. Verify that their sum equals the potential difference across the battery.

SOLUTION:

$$\Delta V_1 = IR_1 = (2.3 \text{ A})(12 \Omega) = 28 \text{ V}$$

$$\Delta V_2 = IR_2 = (2.3 \text{ A})(15 \Omega) = 35 \text{ V}$$

$$\Delta V_3 = IR_3 = (2.3 \text{ A})(5 \Omega) = 12 \text{ V}$$

$$\Delta V_1 + \Delta V_2 + \Delta V_3 = 28 \text{ V} + 35 \text{ V} + 12 \text{ V}$$

$$= 75 \text{ V}$$

= voltage of battery

ANSWER:

Yes, 75 V = voltage of battery.

11. A 22- Ω resistor and a 33- Ω resistor are connected in series and are connected to a 120-V power source.

- What is the equivalent resistance of the circuit?
- What is the current in the circuit?
- What is the potential difference across each resistor?

SOLUTION:

a. $R = R_1 + R_2 = 22 \Omega + 33 \Omega = 55 \Omega$

b.

$$I = \frac{\Delta V}{R} = \frac{120 \text{ V}}{55 \Omega} = 2.2 \text{ A}$$

c.

$$\Delta V_1 = IR_1$$

$$= \left(\frac{\Delta V}{R} \right) R_1$$

$$= \left(\frac{120 \text{ V}}{55 \Omega} \right) (22 \Omega)$$

$$= 48 \text{ V}$$

$$\Delta V_2 = IR_2 = \left(\frac{120 \text{ V}}{55 \Omega} \right) (33 \Omega) = 72 \text{ V}$$

ANSWER:

a. $R = 55 \Omega$

b. $I = 2.2 \text{ A}$

c. $\Delta V_1 = 48 \text{ V}$, $\Delta V_2 = 72 \text{ V}$